

Experiment 1

Linear and Nonlinear Elements

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

.....

Set V power supply = 4 Volts

Carbon Resistor		Si Diode		Light bulb (low currents)		Light Bulb (high currents)	
V (Volts)	I (mA)	V (Volts)	I (mA)	V (Volts)	I (mA)	V (Volts)	I (mA)
0.1		0.10		0.010		0.5	
0.4		0.20		0.02		1.0	
0.8		0.30		0.03		1.5	
1.2		0.40		0.04		2.0	
1.5		0.50		0.05		2.5	
1.8		0.55		0.06		3.0	
2.1		0.61					
2.4		0.64					
2.7		0.67					
3.0		0.70					
3.3		0.73					
3.5		0.76					

Experiment 2

Impedance Matching and Internal Resistance

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

Set V power supply = 8 Volts

R_L (K Ω)	I (mA)	I^{-1} (mA) $^{-1}$	I^2 (mA) 2	$P_L = I^2 R_L$ (mW)
0.10				
0.15				
0.30				
0.60				
0.70				
0.85				
0.90				
0.95				
1.00				
1.05				
1.10				
1.20				
1.50				
2.00				
2.00				
4.00				
8.00				
15.0				
30.0				
60.0				

Experiment 3

Room 253 – Network analysis 1: The SPP and Kirchhoff's law

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____


Instructors Name: _____ Section No.: _____

Date: _____

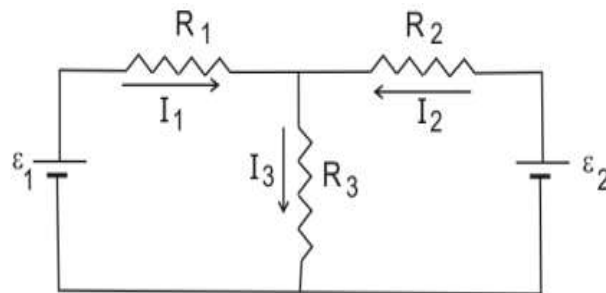1) Kirchhoff's Laws

Connect the circuit shown:

$R_1 = 1 \text{ k}\Omega$,
 $R_2 = 3.3 \text{ k}\Omega$,
 $R_3 = 6.2 \text{ k}\Omega$,
 $\varepsilon_1 = 9 \text{ V}$,
 $\varepsilon_2 = 5 \text{ V}$.




Measure the currents:

	experiment	calculation
I_1 (mA)		
I_2 (mA)		
I_3 (mA)		

2) Superposition Principle


A) Connect the circuit shown:

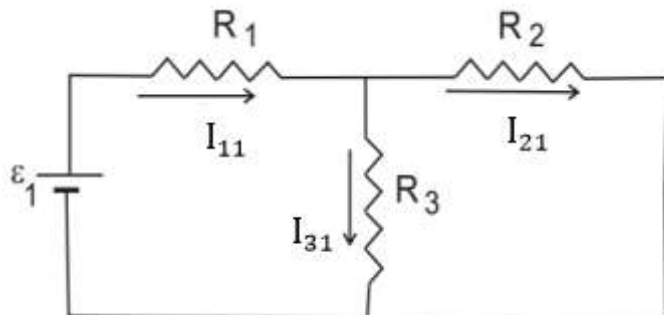

Measure the currents:

	experiment	calculation
I_{11} (mA)		
I_{21} (mA)		
I_{31} (mA)		

B) Connect the circuit shown:

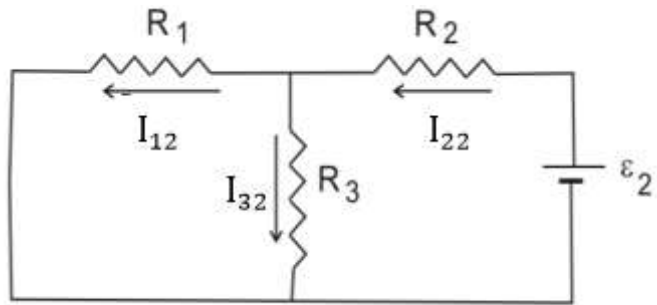

Measure the currents:

	experiment	calculation
I_{12} (mA)		
I_{22} (mA)		
I_{32} (mA)		

C) Find the current using SPP

$I_1 =$

$I_2 =$

$I_3 =$

Experiment 3

Room 263 – Network analysis 1: The SPP and Kirchhoff's law

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____


Instructors Name: _____ Section No.: _____

Date: _____

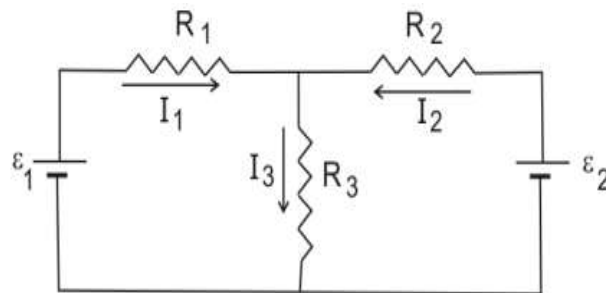1) Kirchhoff's Laws

Connect the circuit shown:

$R_1 = 1 \text{ k}\Omega$,
 $R_2 = 2.2 \text{ k}\Omega$,
 $R_3 = 5.1 \text{ k}\Omega$,
 $\varepsilon_1 = 8 \text{ V}$,
 $\varepsilon_2 = 4 \text{ V}$.




Measure the currents:

	experiment	calculation
I_1 (mA)		
I_2 (mA)		
I_3 (mA)		

2) Superposition Principle


A) Connect the circuit shown:

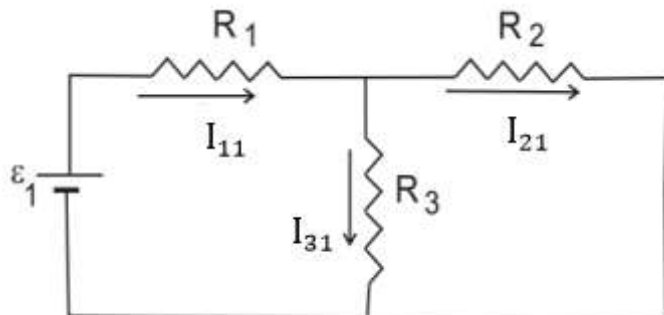

Measure the currents:

	experiment	calculation
I_{11} (mA)		
I_{21} (mA)		
I_{31} (mA)		

B) Connect the circuit shown:

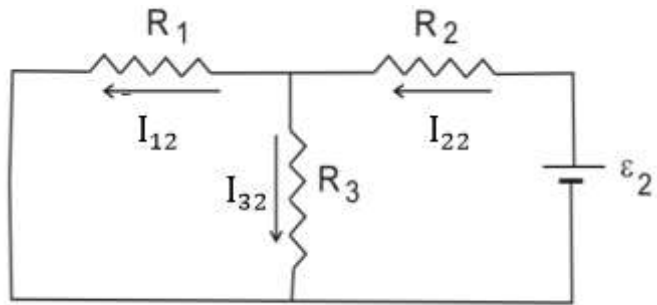

Measure the currents:

	experiment	calculation
I_{12} (mA)		
I_{22} (mA)		
I_{32} (mA)		

C) Find the current using SPP

$I_1 =$

$I_2 =$

$I_3 =$

Experiment 4

Room253–Network analysis 2: Thevenin and Norton technique

Student's Name: _____ Student's No.: _____


Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

Connect the circuit shown:

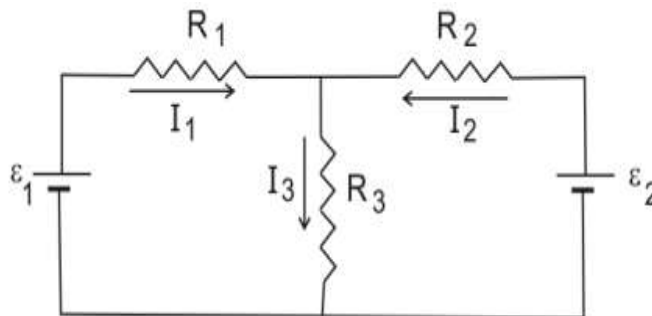$R_1 = 1 \text{ k}\Omega$,
 $R_2 = 3.3 \text{ k}\Omega$,
 $R_3 = 6.2 \text{ k}\Omega$,
 $\varepsilon_1 = 10 \text{ V}$,
 $\varepsilon_2 = 5 \text{ V}$.



A) When $I_1 = I_L$

1) Fill the following table:

	experiment	calculation
R_{eq1}		
ε_{eq1}		
I_{eq1}		

2) Construct **Thevenin** equivalent circuit:

	experiment	calculation
$I_{L1} \text{ (mA)}$		

3) Construct **Norton** equivalent circuit

	experiment	calculation
$I_{L1} \text{ (mA)}$		

B) When $I_3 = I_L$

1) Fill the following table:

	experiment	calculation
R_{eq3}		
\mathcal{E}_{eq3}		
I_{eq3}		

2) Construct **Thevenin** equivalent circuit:

	experiment	calculation
I_{L3} (mA)		

3) Construct **Norton** equivalent circuit

	experiment	calculation
I_{L3} (mA)		

Experiment 4

Room263–Network analysis 2: Thevenin and Norton technique

Student's Name: _____ Student's No.: _____


Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

Connect the circuit shown:

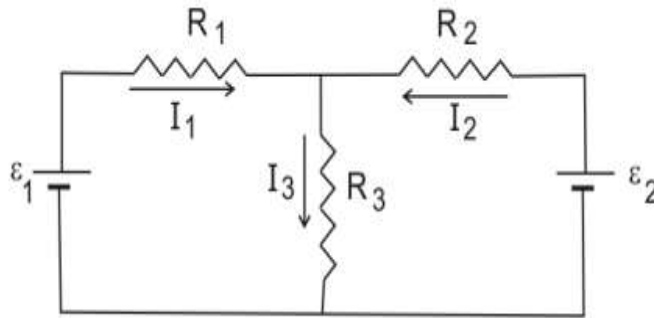$R_1 = 1 \text{ k}\Omega$,
 $R_2 = 2.2 \text{ k}\Omega$,
 $R_3 = 5.1 \text{ k}\Omega$,
 $\varepsilon_1 = 8 \text{ V}$,
 $\varepsilon_2 = 4 \text{ V}$.



A) When $I_1 = I_L$

1) Fill the following table:

	experiment	calculation
R_{eq1}		
ε_{eq1}		
I_{eq1}		

2) Construct **Thevenin** equivalent circuit:

	experiment	calculation
$I_{L1} \text{ (mA)}$		

3) Construct **Norton** equivalent circuit

	experiment	calculation
$I_{L1} \text{ (mA)}$		

B) When $I_3 = I_L$

1) Fill the following table:

	experiment	calculation
R_{eq3}		
\mathcal{E}_{eq3}		
I_{eq3}		

2) Construct **Thevenin** equivalent circuit:

	experiment	calculation
I_{L3} (mA)		

3) Construct **Norton** equivalent circuit

	experiment	calculation
I_{L3} (mA)		

EXPERIMENT 5

DSO

No data sheet

EXPERIMENT 6
CAPACITORS AND INDUCTORS

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____



Date: _____

R=1kΩ

C=find best value for you= _____

L=10mH

Part1: RC-circuit

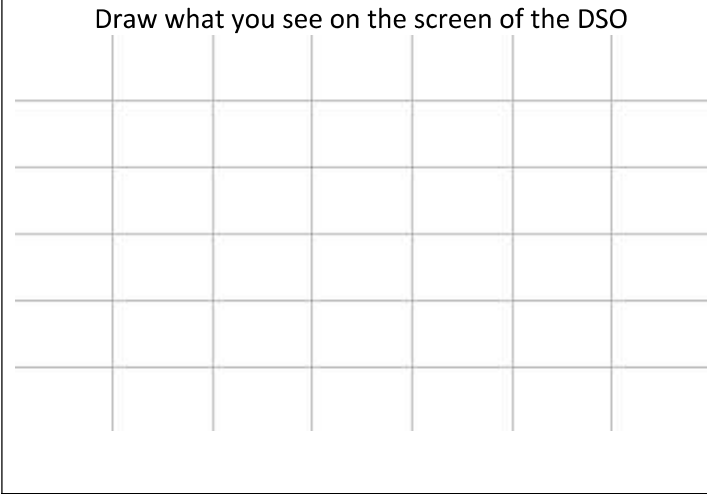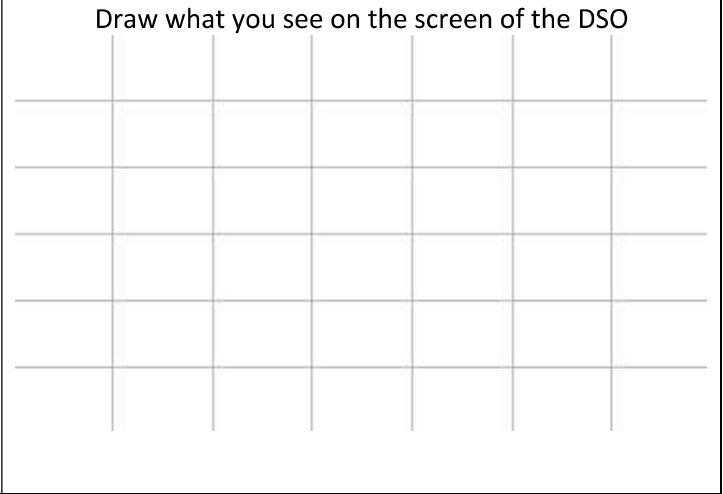Show V_c on the DSO		Show V_R on the DSO	
Draw what you see on the screen of the DSO		Draw what you see on the screen of the DSO	
			
Find $\tau_c =$	Find $\tau_d =$		
$\tau_{exp} =$		$\tau_{theo} =$	

Part2: LR-circuit

Show V_L on the DSO		Show V_R on the DSO	
Draw what you see on the screen of the DSO		Draw what you see on the screen of the DSO	
Find $\tau_c =$		Find $\tau_d =$	
$\tau_{exp} =$		$\tau_{theo} =$	

Part 3: LC-circuit

Show V_c on the DSO		
Draw what you see on the screen of the DSO		
Resonance frequency	$f_{exp} =$	$\omega_{exp} =$
	$f_{theo} =$	$\omega_{theo} =$

Experiment 7

Damped Oscillations

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

.....

C = find best value = _____ L = 10 mH f = (300 – 1000) Hz

-Data:

Part (1): Critical-Damping

Show V_C on the DSO									
Draw what you see on the screen of the DSO									
$R_{\text{Critical}} =$									
$t_1 =$ \bar{z}_{exp}					$\delta_{\text{C,Exp}} =$				

Part (2):Over-Damping

Show V_C on the DSO									
Draw what you see on the screen of the DSO									
$R_{Over} =$									
$t_1 =$ \bar{z}_{exp}					$\delta_{C,Exp} =$				

Part (3):Under-Damping

Show V_C on the DSO									
Draw what you see on the screen of the DSO									
$R_{under} =$									
$t_1 =$ \bar{z}_{exp}									
$\delta_{C,exp} =$									
$f'_{exp} =$					$f'_{theo} =$				

EXPERIMENT 8

Impedance and Reactance

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

C = 0.05 μ F

L = 10 mH

R = 1 k Ω

$f(kHz)$	Δt	ω	$\Phi = \omega \Delta t$
0.2			
0.4			
0.8			
1.6			
3.0			
4.0			
5.0			
6.0			
6.5			
7.0			
7.5			
9.0			
15			
30			
50			
70			
99			

Experiment 9

Resonance

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

L=10mH;

C=0.05 μ F;

R=1k Ω

V_{pp}= 8 Volts

	$R = 600\Omega$		$R = 1.2k\Omega$	
$f(kHz)$	$V_0(volt)$	$I_0(mA)$	$V_0(volt)$	$I_0(mA)$
0.4				
0.6				
0.8				
1.0				
1.5				
3.0				
4.5				
6.0				
7.0				
8.0				
9.0				
15				
30				
60				
90				

Experiment 10

Filters

Student's Name: _____ Student's No.: _____

Partner's Name: _____ Partner's No.: _____

Instructors Name: _____ Section No.: _____

Date: _____

$R = 1\text{ k}\Omega$

$C = 0.07\mu\text{F}$

$V_{\text{inrms}} = 4\text{ Volt}$

-Data:

		Low-pass filter		High-pass filter	
ω (rad/sec)	f (kHz)	V_{Out} (Volt)	A	V_{Out} (Volt)	A
1884					
3768					
5024					
6280					
8792					
10048					
11304					
12560					
14444					
16328					
18840					
21980					
25120					
31400					
62800					
94200					

Type	Low-pass filter acts as integrator when $\omega \gg \omega_{-3dB}$	High-pass filter acts as differentiator when $\omega \ll \omega_{-3dB}$
Square wave		
Saw wave		
Sine wave		

