



BIRZEIT UNIVERSITY
Physics Department

Physics 112

Experiment No. 2

Impedance Matching and Internal Resistance

Student's Name: Mohammad Sheikh Student's No.: 1221541

Partner's Name: Mousa Suhaib Partners' No.: 1210143

Instructor: Shayma' Salama

Section No.: 6

Date: 12-11-2023

➤ Abstract :

- **The aim :** To find the value of the load resistance R_L that satisfies the condition of the maximum power transfer which is $R_L = R + r_{in}$.
- **The method :** The direct calculation of the electrical current passing through a simple circuit at different values of the resistance so we start making the circuit and connecting their elements with each other, we connect a battery that have a voltage of a 10 volts “E” with a constant resistor of $1000\ \Omega$ “R” and then connect the constant resistor with the adjustable resistor “ R_L ” that is the load resistor.
- **The main Result :**
 - **From graph 1 ($1/I$ vs R_L):**
Slope of line = $1/E = 0.0996$.
 $E = 1/\text{Slope} = 10.03\ \text{volt}$.
y-intercept = $\sum R/E = 0.092\ \text{mA}^{-1} = 92.6\ \text{A}^{-1}$.
 $\sum R = (R + r_{in}) = 922\ \Omega$.
 - **From graph 2 (P vs R_L) :**
 $P_{\max} = 24.9001\ \text{mW}$.
 $R_L = (R + r_{in}) = (1\ \text{K}\ \Omega) = 1000\ \Omega$.
- **Introduction :**


A voltage source is characterized by its electromotive force and the maximum value of the current it can deliver to short circuit .

In this experiment, it was expected to measure the internal resistance of the voltage, the potential difference , and the maximum value of the power. This would be done by graphing two graphs, where one is expected to be a linear graph of R_L vs I^{-1} , and the second is expected to have a graph where the maximum value of the power, is known.

➤ Data


R_L (K)	I (ma)	I^{-1}	I^2	$P_L = I^2 R_L$
0.1	9	0.11111111	81	8.1
0.3	7.63	0.1310616	58.2169	17.46507
0.5	6.62	0.1510574	43.8244	21.9122
0.7	5.85	0.17094017	34.2225	23.95575
0.9	5.24	0.19083969	27.4576	24.71184
1	4.99	0.2004008	24.9001	24.9001
1.1	4.75	0.21052632	22.5625	24.81875
1.3	4.34	0.23041475	18.8356	24.48628
1.5	4	0.25	16	24
2	3.34	0.2994012	11.1556	22.3112
2.5	2.86	0.34965035	8.1796	20.449
3	2.5	0.4	6.25	18.75
5	1.67	0.5988024	2.7889	13.9445
8	1.11	0.9009009	1.2321	9.8568
10	0.9	1.11111111	0.81	8.1
20	0.47	2.12765957	0.2209	4.418
50	0.19	5.26315789	0.0361	1.805

➤ Data Analysis :

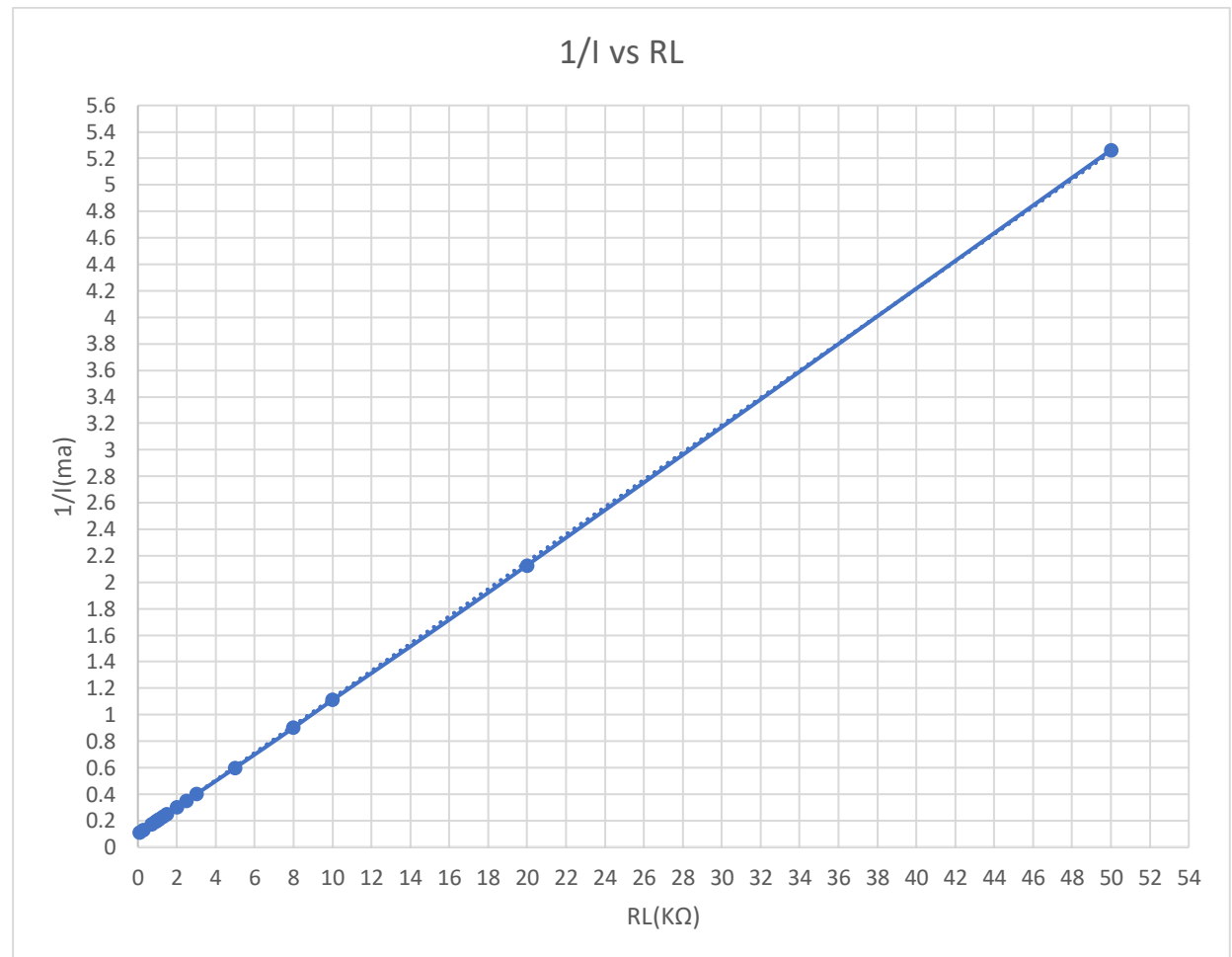

✓ Calculations of Graph 1 :

- Slope = $\frac{\Delta 1/I}{\Delta R} = \frac{0.4 - 0.131}{3 - 0.3} = 0.0996$
- $E = 1/(\text{Ans before rounding}) = 10.03 \text{ volt.}$
- y-intercept = $\Sigma R/E = 0.092 \text{ mA}^{-1} = 92.6 \text{ A}^{-1}.$
- $\Sigma R = (R + r_{in}) = \text{y-intercept} * E = (0.092 * 10.03) = 0.9227 \text{ volt / mA}$
 $= 922 \Omega .$
- $r_{in} = \Sigma R - R$ (where R is $1 \text{ K}\Omega$ making it 1000).
 $r_{in} = 922 - 1000 = -78 \Omega .$

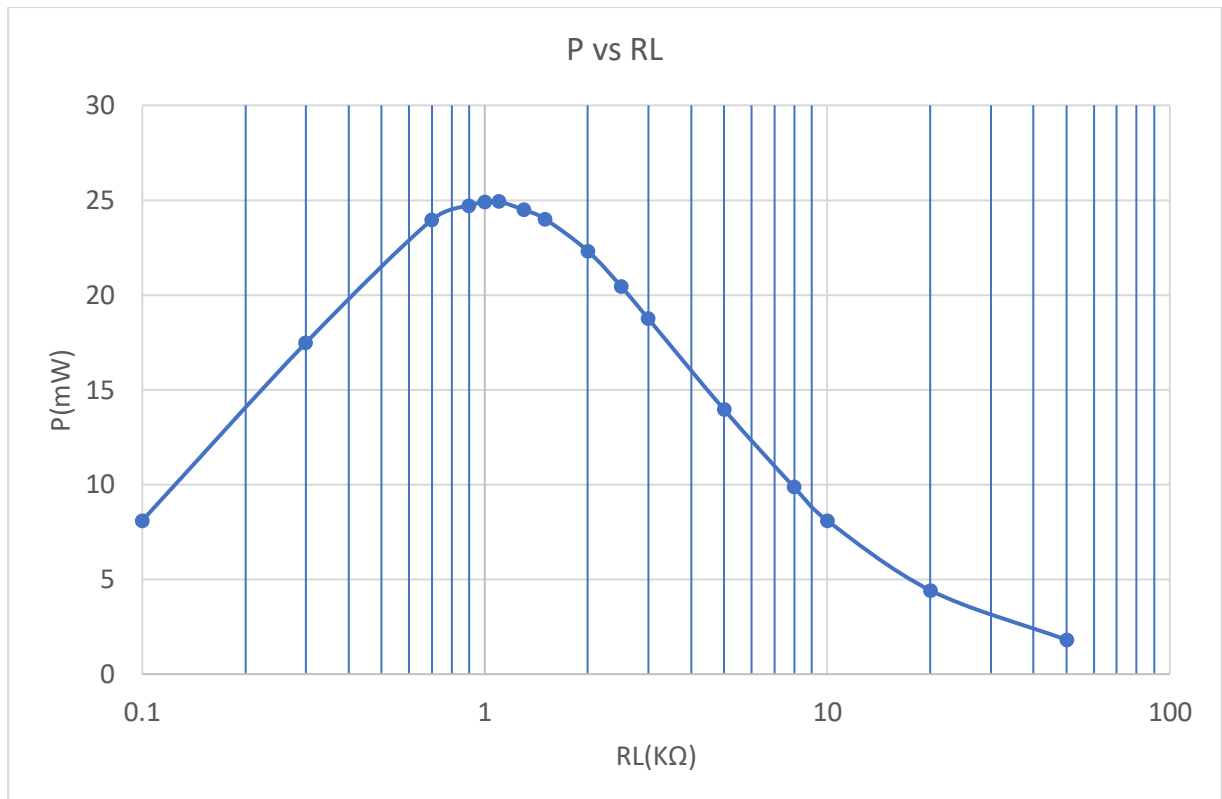

✓ Calculations of Graph 2 :

- We see from figure (power versus resistance) that the maximum value for p occurs at R_L equal (1) $K\Omega \Rightarrow p_{\max}$ equal (24.9001) mW .
- **And the maximum power is when :**
 $R_L = (R + r_{in}) = (1k\ K\Omega) = (1000\ \Omega)$.
 $R_{in} = R_L - R = 1000 - 1000 = 0\ \Omega$

➤ Result and conclusion :

- There should be an internal resistance in every circuit .
- To reach the maximum value of the power transferring the load resistance should be equal to the sum of the additional resistance and the internal resistance.
- Our Result of $(R + r_{in})$ from Linear graph = $922\ \Omega$ and $(R + r_{in})$ from semi log = $1000\ \Omega$.
 We noticed that difference in values of $(R + r_{in})$ that occurred due to Systemetic errors and random errors.